Electricity

TRY YOURSELF

ANSWERS

....

 \Rightarrow

1. The physical quantity coulomb/second is called electric current.

2. Conventional current in the direction of flow of positive charge.

3. (b) : As we know that, work done, $W = qV = 0.5 \times 20$ = 10 J

4. (b) : Work done in moving an unit charge across two points in an electric circuit is a measure of potential difference.

5. S.I. unit of potential difference is volt.

6. (b) : If area of cross-section is halved, then, resistance becomes,

 $R' = \rho \frac{l}{A'} = \rho \frac{l}{A/2} = \frac{2\rho l}{A} = 2R$

(Taking length remains in changed)

So, the resistance increases two times of its original.

7. Resistance of a pure metal increases with rise in temperature.

8. S.I. unit of resistivity is ohm-meter (Ω -m).

9. By combining two resistors each of 2 Ω in parallel and then their equivalent with other 2 Ω resistor we can obtain 3 Ω resistance.



10. (b) : In homes electrical devices are connected in parallel.

11. (b) : If the potential difference across each resistor is same then the resistors are connected in parallel.

12. (b) : If a current of 3.5 A flows through a hair dryer, then for normal use of fuse with rating 5 A will be most suitable among given options.

13. Given, power of the lamp, P = 25 W and voltage, V = 200 V.

Power,
$$P = VI$$

 $I = \frac{P}{V} = \frac{25 \text{ W}}{200 \text{ V}} = \frac{1}{8} \text{ A} = 0.125 \text{ A}$

MtG BEST SELLING BOOKS FOR CLASS 10

10

NCERT

F⁴NGERTIPS

MATHEMATICS



10





















Visit www.mtg.in for complete information